

# Binary-to-BCD Converter

# Shift and Add-3 Algorithm

1. Shift the binary number left one bit.
2. If 8 shifts have taken place, the BCD number is in the *Hundreds, Tens, and Units* column.
3. If the binary value in any of the BCD columns is 5 or greater, add 3 to that value in that BCD column.
4. Go to 1.

Operation	Hundreds	Tens	Units	Binary							
HEX				F				F			
Start				1	1	1	1	1	1	1	1

## Steps to convert an 8-bit binary number to BCD

Operation	Hundreds	Tens	Units	Binary			
B				7	4	3	0
HEX				<b>F</b>		<b>F</b>	
Start				1 1 1 1	1 1 1 1		
Shift 1			1	1 1 1 1	1 1 1		
Shift 2			1 1	1 1 1 1	1 1		
Shift 3			1 1 1	1 1 1 1	1		
Add 3			1 0 1 0	1 1 1 1	1		
Shift 4		1	0 1 0 1	1 1 1 1			
Add 3		1	1 0 0 0	1 1 1 1			
Shift 5		1 1	0 0 0 1	1 1 1			
Shift 6		1 1 0	0 0 1 1	1 1			
Add 3		1 0 0 1	0 0 1 1	1 1			
Shift 7	1	0 0 1 0	0 1 1 1	1			
Add 3	1	0 0 1 0	1 0 1 0	1			
Shift 8	1 0	0 1 0 1	0 1 0 1				
BCD	<b>2</b>	<b>5</b>	<b>5</b>				
P	9 8	7 4	3 0				
z	17 16	15 12	11 8	7	4	3	0



# Example of converting hex E to BCD

Operation	Tens	Units	Binary
HEX			E
Start			1 1 1 0
Shift 1		1	1 1 0
Shift 2		1 1	1 0
Shift 3		1 1 1	0
Shift 4		1 1 1 0	
6		0 1 1 0	
Add 6	1	0 1 0 0	
BCD	1	4	

```
-- Title: Binary-to-BCD Converter
```

```
library IEEE;
```

```
use IEEE.std_logic_1164.all;
```

```
use IEEE.std_logic_unsigned.all;
```

```
entity binbcd is
```

```
    port (
```

```
        B: in STD_LOGIC_VECTOR (7 downto 0);
```

```
        P: out STD_LOGIC_VECTOR (9 downto 0)
```

```
    );
```

```
end binbcd;
```

```
architecture binbcd_arch of binbcd is
```

```
begin
```

```
  bcd1: process (B)
```

```
    variable z: STD_LOGIC_VECTOR (17 downto 0);
```

```
  begin
```

```
    for i in 0 to 17 loop
```

```
      z(i) := '0';
```

```
    end loop;
```

```
    z(10 downto 3) := B;
```

```
    for i in 0 to 4 loop
```

```
      if z(11 downto 8) > 4 then
```

```
        z(11 downto 8) := z(11 downto 8) + 3;
```

```
      end if;
```

```
      if z(15 downto 12) > 4 then
```

```
        z(15 downto 12) := z(15 downto 12) + 3;
```

```
      end if;
```

```
      z(17 downto 1) := z(16 downto 0);
```

```
    end loop;
```

```
    P <= z(17 downto 8);
```


```
  end process bcd1;
```

```
end binbcd_arch;
```

Operation	Hundreds	Tens	Units	Binary			
B				7	4	3	0
HEX				F		F	
Start				1	1	1	1
Shift 1			1	1	1	1	1
Shift 2			1	1	1	1	1
Shift 3			1	1	1	1	1
Add 3			1	0	1	1	1
Shift 4		1	0	1	0	1	1
Add 3		1	1	0	0	0	0
Shift 5		1	1	0	0	0	1
Shift 6		1	1	0	0	1	1
Add 3		1	0	0	1	1	1
Shift 7	1	0	0	1	0	1	1
Add 3	1	0	0	1	0	1	0
Shift 8	1	0	0	1	0	1	0
BCD	2	5	5				
P	9	8	7	4	3	0	
z	17	16	15	12	11	8	7



# 16-bit Binary-to-BCD Converter

 

# Verilog *binbcd*

```

module binbcd(B,P);


  input [15:0] B;

  output [15:0] P;

  reg [15:0] P;

  reg [31:0] z;

  integer i;
  
```

 




```

always @(B)
begin
    for(i = 0; i <= 31; i = i+1)
        z[i] = 0;
    z[18:3] = B;

    for(i = 0; i <= 12; i = i+1)
    begin
        if(z[19:16] > 4)
            z[19:16] = z[19:16] + 3;
        if(z[23:20] > 4)
            z[23:20] = z[23:20] + 3;
        if(z[27:24] > 4)
            z[27:24] = z[27:24] + 3;
        if(z[31:28] > 4)
            z[31:28] = z[31:28] + 3;
        z[31:1] = z[30:0];
    end

    P = z[31:16];
end
endmodule

```

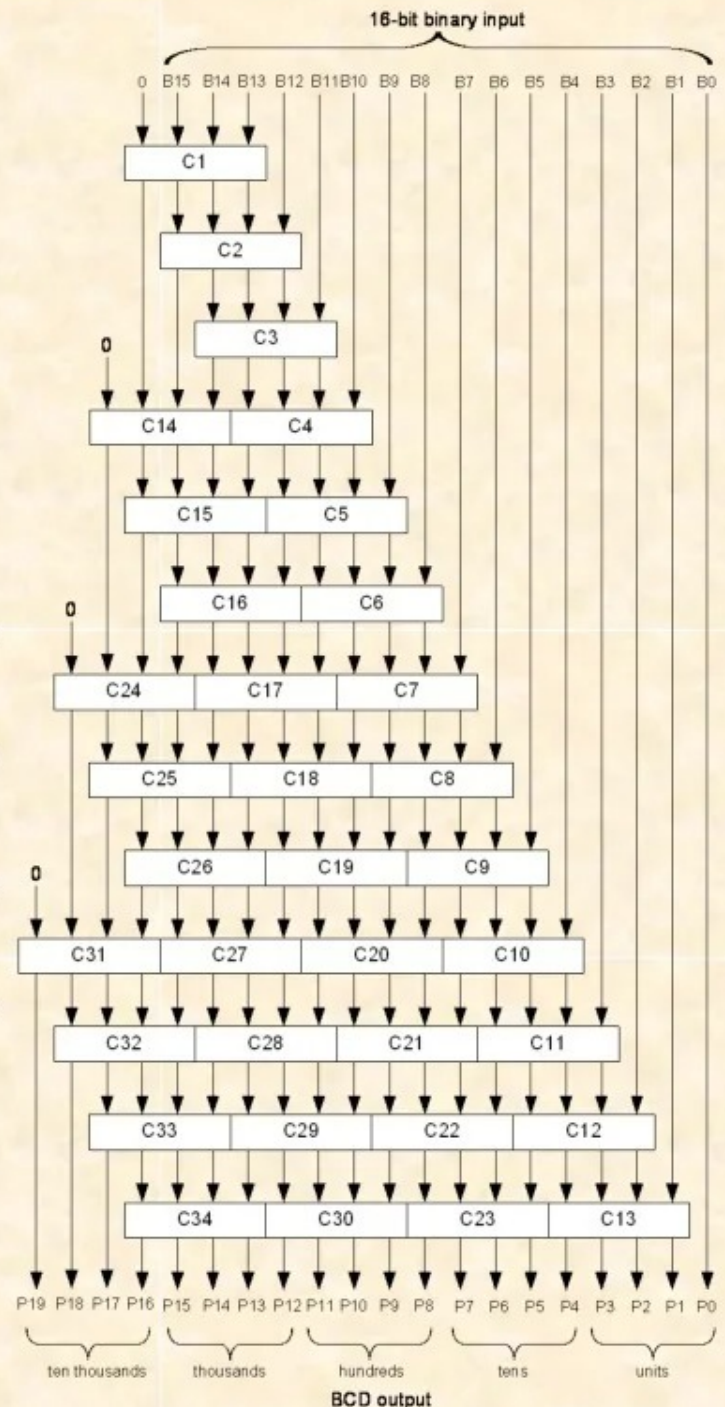

## Steps to convert a 6-bit binary number to BCD

1. Clear all bits of  $z$  to zero
2. Shift  $B$  left 3 bits  
 $z[8:3] = B[5:0];$
3. Do 3 times  
     if  $Units > 4$  then add 3 to  $Units$   
     (note:  $Units = z[9:6]$ )  
     Shift  $z$  left 1 bit
4.  $Tens = P[6:4] = z[12:10]$   
 $Units = P[3:0] = z[9:6]$

Operation	Tens		Units		Binary					
<b>B</b>					5	4	3	2	1	0
<b>HEX</b>					3				F	
<b>Start</b>					1	1	1	1	1	1
<b>Shift 1</b>				1	1	1	1	1	1	
<b>Shift 2</b>				1	1		1	1	1	
<b>Shift 3</b>				1	1	1		1	1	
<b>Add 3</b>				1	0	1	0		1	
<b>Shift 4</b>		1		0	1	0	1		1	
<b>Add 3</b>		1		1	0	0	0		1	
<b>Shift 5</b>		1	1	0	0	0	1		1	
<b>Shift 6</b>		1	1	0	0	1	1			
<b>BCD</b>		6		3						
<b>P</b>	7	4	3	0						
<b>z</b>	13	10	9	6	5					0

Example of Verilog code for 16-bit conversion is shown on Slide 9

Example of VHDL code for 8-bit conversion is shown on Slide 6